
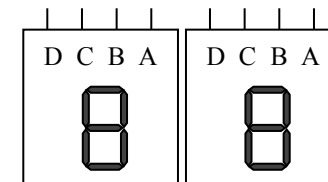
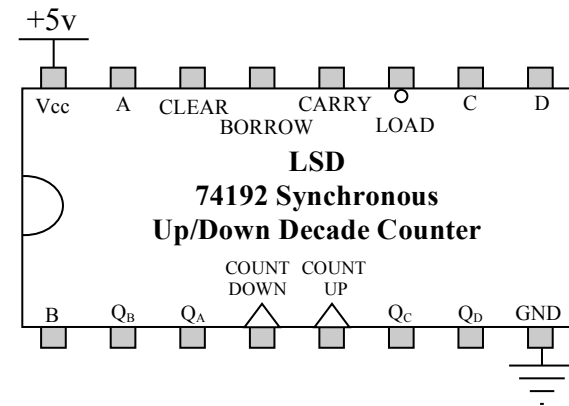
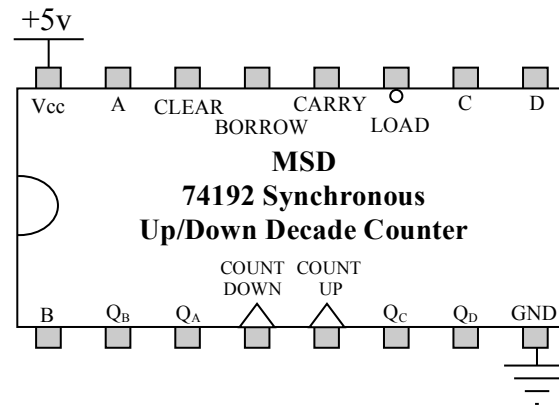
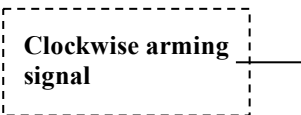
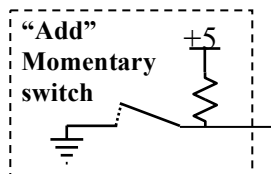
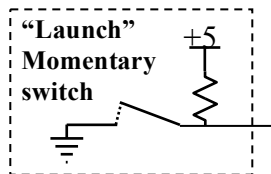


Name: _____

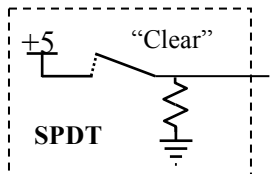Your circuit: (Do not include motor circuit, but answer questions 1. _____, 2. _____, and 3. _____)



- (→) "Full
- (→) "Som
- (→) "Empty