

Quiz #5: Ohm's Law

Name: _____

For the circuit shown, you know that:

$$R_1 = 400 \, \Omega$$


$$R_2 = 300 \, \Omega$$

$$R_3 = 1200 \, \Omega$$

Also, you know that the current through resistor 2 is:

$$I_2 = 10.0 \, \text{mA}$$

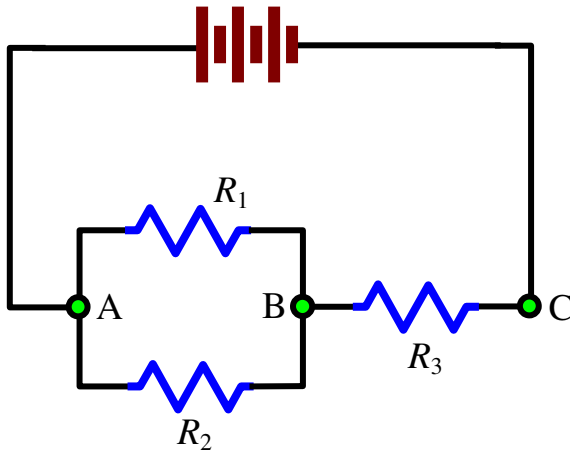Determine the five quantities that are listed in the box.



- | |
|---------------------|
| $V_A - V_B =$ |
| I through $R_1 =$ |
| I through $R_3 =$ |
| $V_B - V_C =$ |
| $V_A - V_C =$ |