

Name: \_\_\_\_\_

Date: \_\_\_\_\_

Partner: \_\_\_\_\_

Part 1) Value of your capacitor:  $C =$  \_\_\_\_\_ nF

Value of your resistor:  $R =$  \_\_\_\_\_ k $\Omega$

Amplitude of your function generator:  $V_0 =$  \_\_\_\_\_ V

Time constant of circuit:  $\tau =$  \_\_\_\_\_ ms

Part 2) Frequency of your function generator:  $f =$  \_\_\_\_\_ kHz

Period of your function generator:  $T =$  \_\_\_\_\_ ms

Part 3) Scope setting:  $vertical =$  \_\_\_\_\_ volts/div

Scope setting:  $horizontal =$  \_\_\_\_\_ ms/div

Amplitude cursors:  $V_{pp} =$  \_\_\_\_\_ V

Time cursors: time when  $V = V_{pp}/e$   $\tau =$  \_\_\_\_\_ ms

Part 4) New value of capacitor:  $C =$  \_\_\_\_\_ nF

New time constant of circuit:  $\tau =$  \_\_\_\_\_ ms

New frequency of your function generator:  $f =$  \_\_\_\_\_ kHz

**Linest results: Discharging**

**Attach ONE sheet having both plots,  
professionally formatted.**

Units $\rightarrow$		

Part 5) New frequency of your function generator:  $f =$  \_\_\_\_\_ kHz

New time constant of circuit:  $\tau =$  \_\_\_\_\_ ms

Apparent resistance:  $R =$  \_\_\_\_\_  $\Omega$

Part 6) Test capacitance:  $C =$  \_\_\_\_\_ nF