

## Physics 125: Analytical Physics II

### “No Risk” Quiz


In the circuit shown, the capacitors have values

$$C_1 = 3 \mu\text{F}$$

$$C_2 = 6 \mu\text{F}$$

$$C_3 = 2 \mu\text{F}$$

$$C_4 = 4 \mu\text{F}$$

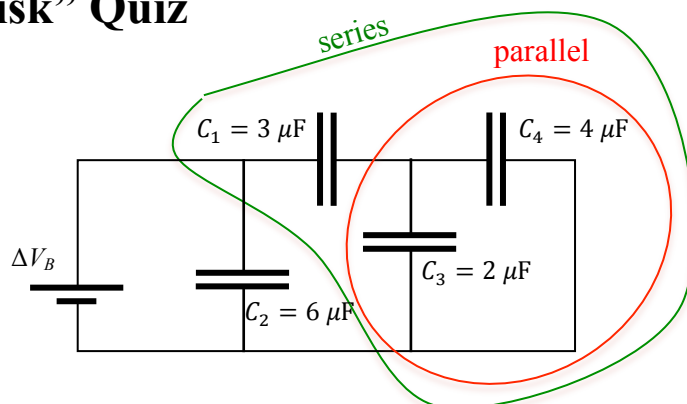

The power supply is set to  $V_B = 24 \text{ V}$ .

(a) Circle any groups of *individual* capacitors that can be considered either “in parallel” or “in series,” and label them. (You *may* then circle how that/those equivalent capacitors combine with others, but that will not be graded.) **Only 3&4 in parallel. 1 & 2 can't be combined with any other single capacitor.**

(b) Once all resulting currents stop flowing, what is the charge on capacitor  $C_4$ ?

First, work our way out:

- $C_{34} = C_3 + C_4 = 6\mu\text{F}$  (parallel)
- $1/C_{134} = 1/C_1 + 1/C_{34} = \frac{1}{3\mu\text{F}} + \frac{1}{6\mu\text{F}} = \frac{1}{2\mu\text{F}} \rightarrow C_{134} = 2\mu\text{F}$  (series)
- $C_{1234} = C_2 + C_{134} = 8\mu\text{F}$  (parallel)

Then, work our way back in:

- $\Delta V_B = \Delta V_2 = \Delta V_{134}$  (parallel) so that we really didn't need to worry about the 2+134 combination after all
- 1 and 34 in series:  $Q_1 = Q_{34} = Q_{134} = C_{134}\Delta V_{134} = 2\mu\text{F} \cdot 24\text{V} = 48\mu\text{C}$
- 3 and 4 in parallel:  $\Delta V_3 = \Delta V_4 = \Delta V_{34} = Q_{34}/C_{34} = 48\mu\text{C}/6\mu\text{F} = 8\text{V}$
- $Q_4 = C_4\Delta V_4 = 4\mu\text{F} \cdot 8\text{V} = 32\mu\text{C}$

There is a shortcut: Parallel capacitors split charge proportionally to their capacitance.  $C_4$  has twice the capacitance of  $C_3$ , so:

$$Q_4 = \frac{2}{3} Q_{34} \text{ and } Q_3 = \frac{1}{3} Q_{34}$$

However, like most shortcuts, this should only be used if you have a very solid understanding of the basic method.

From the Formula Sheet:

$$k = 8.99 \times 10^9 \text{ N} \cdot \text{m}^2/\text{C}^2$$

$$\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2/\text{N} \cdot \text{m}^2$$

$$q = CV$$

$$C = \kappa \frac{\epsilon_0 A}{d}$$

$$C_{\text{eq}} = C_1 + C_2 + C_3 + \dots$$

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$$