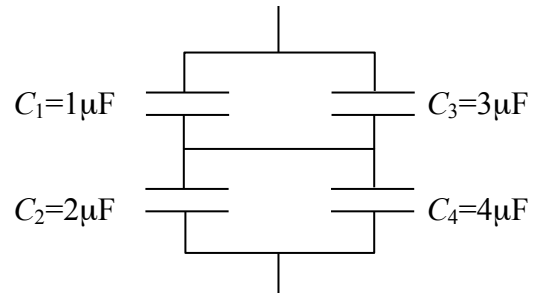


Inside a Network of Capacitors

Here is configuration of capacitors, with some capacitance values. Suppose we apply 12 V top to bottom. What is the charge on cap 2?

Work our way out with equivalent capacitors:

- Top pair are in parallel, $C_{13}=4\mu\text{F}$. Bottom pair are in parallel, $C_{24}=6\mu\text{F}$.
- Those two are in series, $C_{1324}=12/5 \mu\text{F}$



Now work our way back in:

- C_{13} and C_{24} are in series, so we need to use the fact that these equivalent capacitors have the same charge...

- $Q_{1234} = C_{1234} V_{1234} = \left(\frac{12}{5} \mu\text{F}\right)(12\text{V}) = 28.8\mu\text{C}$

- $Q_{24} = Q_{1234} = 28.8\mu\text{C}$ (also = Q_{13} but we don't need that fact for this problem)

- C_2 and C_4 are in parallel, so we need to use the fact that these capacitors have the same potential difference across them...

- $V_{24} = \frac{Q_{24}}{C_{24}} = \frac{28.8\mu\text{C}}{6\mu\text{F}} = 4.8\text{V}$

- $V_2 = V_{24} = 4.8\text{V}$ (also = V_4 but we don't need that fact for this problem)

- Finally, we need the charge on cap 2 instead of voltage,

- $Q_2 = C_2 \Delta V_2 = (2 \mu\text{F})(4.8\text{V}) = 9.6\mu\text{C}$