

Homework #1


Reading Assignment: Chapters 3-1 through 3-9 of *Digital Systems: Principles and Applications*, 10th edition, by Tocci, Widmer & Moss.

1-1 You can't read the number on a chip, but you think it is either a 7408 or a 7432. What one set of inputs can be used to determine which chip it is? Explain your answer. For these inputs, if the result is high, which chip is it?

1-2 Repeat problem 1-1 if the chip is either a 7400 or a 7486.

1-3 Repeat problem 1-1 if the chip is either a 7432 or a 7486.

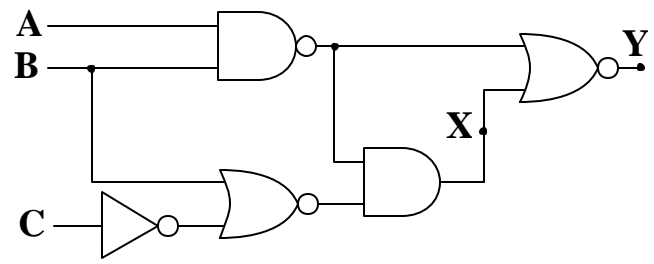1-4 For the circuit shown, determine the Boolean expressions for X and Y, and create a truth table for both.



1-5 A bank alarm A is high (on) if the vault V is open (high), and is also high if an entry door D is high (open) while a key K is high (removed from its hook). Write the Boolean expression and draw the circuit for A.

1-6 Using *Digital Works*, create a circuit as described below. When done, save it as **abc23-assign01.dwm**, where **abc23** is your Geneseo email name. Then, drag it into my inbox (\\files\Inbox\Physics\Pogo).

- a. Create 4 Interactive Inputs, and label them A, B, C, and D using a separate text box, with a bold, size 12 font.
- b. Create 2 output LEDs, and label them Q and R.
- c. Create the circuit such that $Q = \overline{(A+B)}(CD)$, and $R = (B+C)\overline{A}\overline{D}$.
When done, all wires should be neat and either vertical or horizontal.
- d. Add another text box indicating your name.
- e. On paper (i.e., along with parts 1-1 through 1-6 above), complete a truth table for this circuit:

| A | B | C | D | Q | R |
|------|------|------|------|------|------|
| 0 | 0 | 0 | 0 | | |
| 0 | 0 | 0 | 1 | | |
| 0 | 0 | 1 | 0 | | |
| 0 | 0 | 1 | 1 | | |
| 0 | 1 | 0 | 0 | | |
| 0 | 1 | 0 | 1 | | |
| 0 | 1 | 1 | 0 | | |
| etc. | etc. | etc. | etc. | etc. | etc. |
| | | | | | |
| | | | | | |