

## Homework #4


Reading Assignment: Chapters 9-1 through 9-2, and 5-1 through 5-5 of *Digital Systems: Principles and Applications*, 10<sup>th</sup> edition, by Tocci, Widmer & Moss.

### Decoders:

- 4-1 Consider a 74138 decoder chip with select inputs  $A_2A_1A_0$  and enable inputs  $\overline{E}_2 \overline{E}_1 \overline{E}_0$ . Determine the state of all 8 outputs when:
- all six inputs are low;
  - Five inputs are low, but  $E_3$  is high.
  - Four inputs are high, but  $\overline{E}_2 = \overline{E}_1 = \text{low}$
  - All six inputs are high.

- 4-2 Using only 74138 chips, wires, ground, and Vcc, design a 1-of-16 decoder. There should be four select inputs  $D_3D_2D_1D_0$  and one (active low) enable input  $E_1$ .

 - 4-3 A 74138 decoder has  $\overline{E}_2 = \overline{E}_1 = \text{low}$ . The other four inputs vary as seen in this timing diagram. Redraw these timing diagrams, and lined up below them, draw the outputs  $\overline{O}_0, \overline{O}_3, \overline{O}_6,$  and  $\overline{O}_7$ .



- 4-4 You attempt to wire a 7447 BCD driver to a 7-segment display device. While you expect to see regular numbers from 0 to 9, you instead see the following. Determine what mistake was made during the wiring process.



- 4-5 Repeat problem 4-4 for this output:



### Latches:

- 4-6 A NAND latch starts with  $Q = 0$ . Then, the inputs Set and Reset are varied as seen in this timing diagram. Redraw this diagram, with the output  $Q$  underneath it.
- 4-7 A NOR latch starts with  $Q = 0$ . Then, the inputs Set and Reset are varied as seen in this timing diagram. Redraw this diagram, with the output  $Q$  underneath it.
- 4-8 You want to debounce a SPDT switch using a NOR latch. You of course may also use resistors, ground, and Vcc. Draw the necessary circuit.

