

Part of our goal is not merely to *solve* the ODE, but to find it! Let's find $I_3(t)$.

1. With the switch in the initial position, replace each capacitor with a broken wire, and each inductor with a wire. Use these results to find initial conditions for voltages across capacitors, or for currents through inductors.

In this example: $V_1 = V_0, V_2 = 3V_0, V_3 = V_4 = 0$
 $I_2 = 0, I_1 = I_3 = V_0/4R_1$

Goal: $V_2(0) - V_4(0) = 3V_0$, and $I_3(0) = V_0/4R_1$

2. With the switch in the final position, replace each capacitor and inductor with a source matching step 1. Compute the initial current through each capacitor, and voltage across each inductor! Then convert the results into initial slopes (V' for capacitors, I' for inductors).

In this example: $V_1 = 3/4V_0, V_2 = 11/4V_0, V_3 = -1/4V_0, V_4 = -1/4V_0$
 $I_1 = 0, I_2 = -V_0/4R_1$

Capacitor equation: $I_2 = -V_0/4R_1 = C V_2'(0) - C V_4'(0)$

Inductor equation: $V_3 - 0 = -1/4V_0 = L I_3'(0)$

3. With the switch in the final position, replace each capacitor with a broken wire, and each inductor with a wire. Use these results to find final conditions for voltages across capacitors, or for currents through inductors. This step is needed whenever the ODE is non-homogeneous, so we can find the "particular" solution.

In this example: $V_1 = V_3 = V_4 = 0, V_2 = 2V_0$
 $I_2 = I_3 = 0$

Goal: $V_2(\infty) - V_4(\infty) = 2V_0$, and $I_3(\infty) = 0$

4. With the switch in the final position, write the "real" equations needed to create the 2nd order ODE for time between 0 and ∞ . It's my opinion that it's easier to find an equation for current rather than voltage.

Basic equations: $V_2 = V_1 + 2V_0, V_1 - V_3 = 4R_1 I_3, 0 - V_4 = R_1 I_3,$
 $V_3 - 0 = L I_3', I_3 = C V_4' - C V_2'$

Algebra: A general procedure might be to take first and second derivatives of every resistor equation, a first derivative of every capacitor and every inductor equation,

$C L I_3'' + 5 R_1 C I_3' + I_3 = 0 \quad I_3(0) = V_0/4R_1 \quad I_3'(0) = -V_0/4L$
 ... since this equation is homogeneous for I_3 , we didn't need step 3!

