

Instructions for Measurement and Analysis

You measure the first four columns directly, and compute the last seven. For state, write “on”, “off”, or “sat”. Compute β even when it doesn’t make sense to do so. Before doing the lab, directly examine the output of the LED by eye while varying V_{DD} from 0 to 5V. This will give you a feeling for what “bright” and “dark” mean in the context of this experiment. Do not exceed 5 V! Do not aim the LED directly into your eye; it can be painfully bright!

Post-Analysis Questions:

1. What seems to be the most likely value for β ? Explain your choice.
2. Discuss any cases where it was not perfectly clear whether the state was “on”, “off”, or “sat”. “Discussing” is not the same as “listing”.
3. What would be the impact of choosing a different value of either R_B or R_0 ? Your answer should only address how the changes would affect the primary output (V_C).
4. Since you figured out in the previous question that the value for R_B does not have a significant impact on V_C , and that generally smaller is better, what negative consequences might arise if we simply replaced R_B with a wire?
5. You may have noticed in the table that the input range for V_{DD} is not exactly linear. Why did we skip $V_{DD} = 0.5, 1.0, \text{ and } 1.5$?